

Generic Schematic Checklist

v2012-10-15

- **Visual Design**
 - Power supplies use supply symbols, not wires
 - Positive supplies point up, and negative supplies/ground point down
 - Groups of nets above ≥ 4 nets collected into buses
 - All nets descriptively named
 - Net “stubs” have an “off-sheet” (“XREF” in EAGLE) label
 - Blocks in your schematic clearly labeled
 - There's a frame around the schematic
 - It's clear *where* your power is coming from
 - Data flow (inputs, outputs) are clear and labeled
- **Part values**
 - Special case capacitors marked with power and tolerance
 - Capacitors have the appropriate voltage
 - Power dissipation checked in all of your resistors
 - Special case resistors marked with power and tolerance
 - Print your BOM. Check that each part is in stock at a distributor.
- **Electrical Rule checks**
 - All of your components have values (including “NP”)
 - All inputs have the correct voltage levels
 - All outputs have the correct load impedance
 - All MOSFETs placed **forwards** wrt the body diode
 - **No (non-approved) errors OR warnings in the ERC**
 - Your schematic is peer reviewed by at least two different people.
 - Double check your approved errors, looking for anomalies and possible errors.
- **Best Practices**
 - Small, low ESR (e.g., ceramic) bypass capacitors on ALL IC supplies
 - Large bypass (e.g., electrolytic) capacitors on your board at the power connector and regulator IC.
 - **Design for Test:** place test points on critical signals
 - **Design for Fail:** group components in separable modular blocks
 - Place programming connectors and DOUBLE CHECK their pinouts
 - Add debugging hardware (e.g., test switches, LEDs, scope probe points, etc)